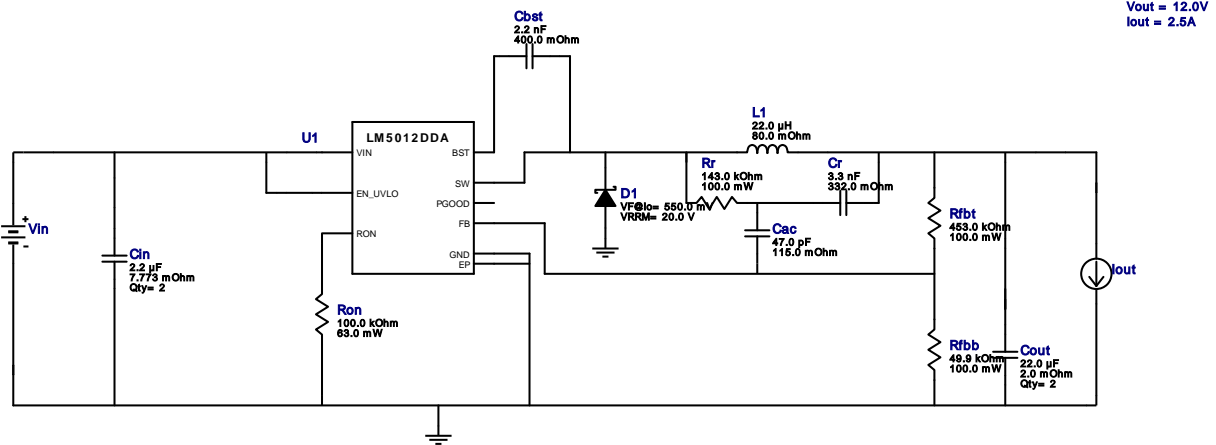


# WEBENCH® Design Report

Design : 2 LM5012DDAR  
LM5012DDAR 15V-85V to 12.00V @ 2.5A

VinMin = 14.0V  
VinMax = 16.0V  
Vout = 12.0V  
Iout = 2.5A

Device = LM5012DDAR  
Topology = Buck  
Created = 2024-04-02 19:28:31.456  
BOM Cost = \$2.59  
BOM Count = 14  
Total Pd = 3.21W



## Design Alerts





### Component Selection Information







If duty cycle is greater than 75% and switching is irregular then please try reducing Resistance Rr.







## Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cac	Kemet	C0805C470J5GACTU Series= C0G/NP0	Cap= 47.0 pF ESR= 115.0 mOhm VDC= 50.0 V IRMS= 505.0 mA	1	\$0.01	 0805 7 mm <sup>2</sup>
Cbst	Kemet	C0805C222K5RACTU Series= X7R	Cap= 2.2 nF ESR= 400.0 mOhm VDC= 50.0 V IRMS= 251.0 mA	1	\$0.01	 0805 7 mm <sup>2</sup>
Cin	MuRata	GRM21BR71E225KA73L Series= X7R	Cap= 2.2 uF ESR= 7.773 mOhm VDC= 25.0 V IRMS= 1.35654 A	2	\$0.14	 0805 7 mm <sup>2</sup>
Cout	MuRata	GRM32ER61E226KE15L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.67 A	2	\$0.23	 1210 15 mm <sup>2</sup>
Cr	Kemet	C0805C332K5RACTU Series= X7R	Cap= 3.3 nF ESR= 332.0 mOhm VDC= 50.0 V IRMS= 319.0 mA	1	\$0.01	 0805 7 mm <sup>2</sup>
D1	Diodes Inc.	B520C-13-F	VF@Io= 550.0 mV VRRM= 20.0 V	1	\$0.21	 SMC 83 mm <sup>2</sup>
L1	Bourns	SDR1105-220ML	L= 22.0 uH 80.0 mOhm	1	\$0.49	 SDR1105 157 mm <sup>2</sup>

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Rfbb	Yageo	RC0603FR-0749K9L Series= ?	Res= 49.9 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
Rfbt	Yageo	RC0603FR-07453KL Series= ?	Res= 453.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
Ron	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
Rr	Vishay-Dale	CRCW0603143KFKEA Series= CRCW..e3	Res= 143.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
U1	Texas Instruments	LM5012DDAR	Switcher	1	\$1.08	DDA0008E-MFG 55 mm <sup>2</sup>

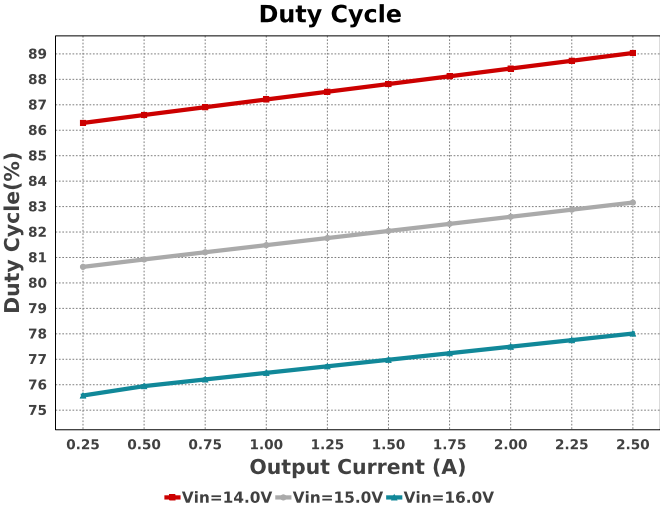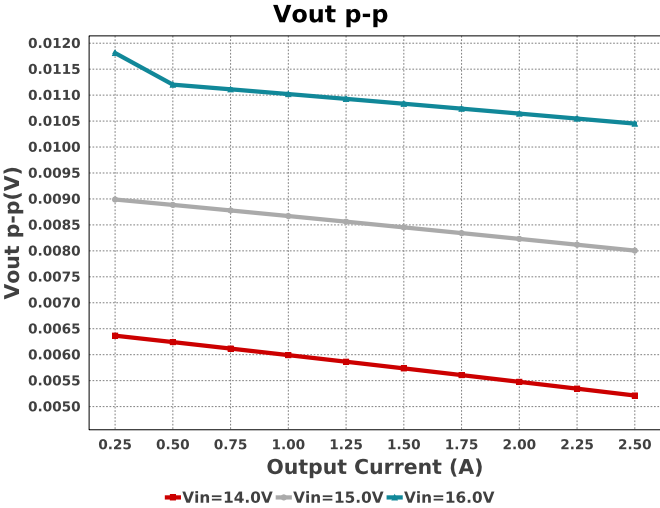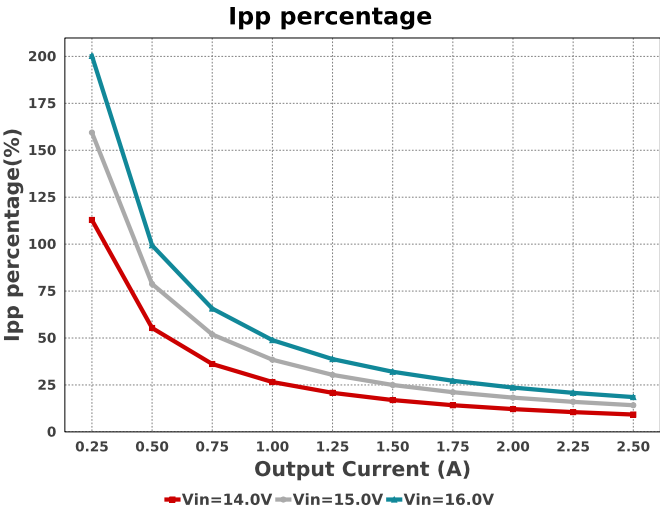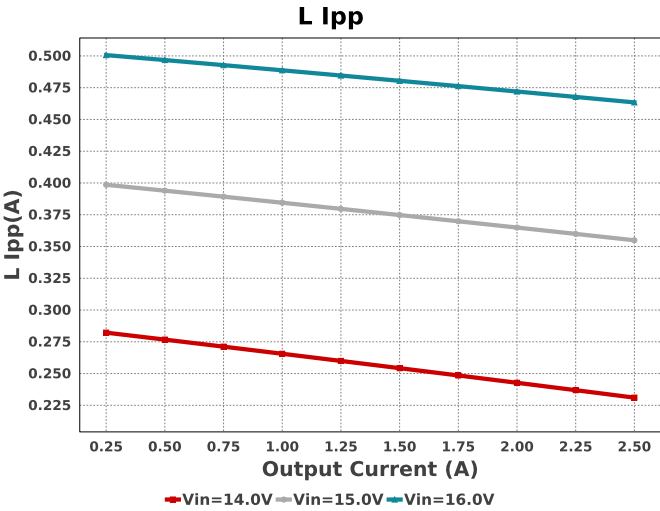

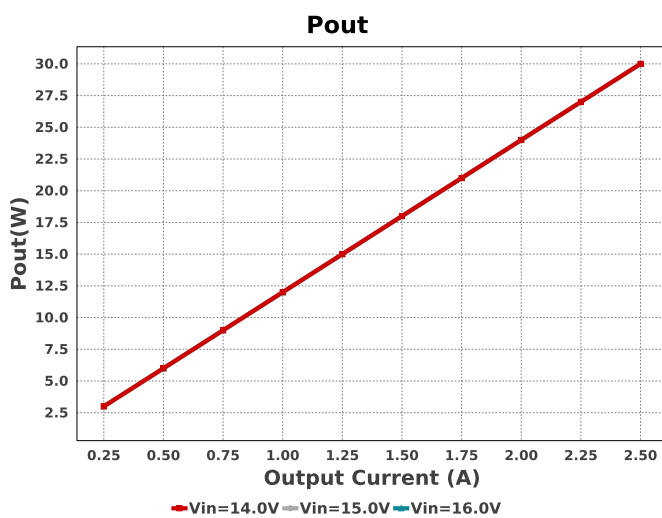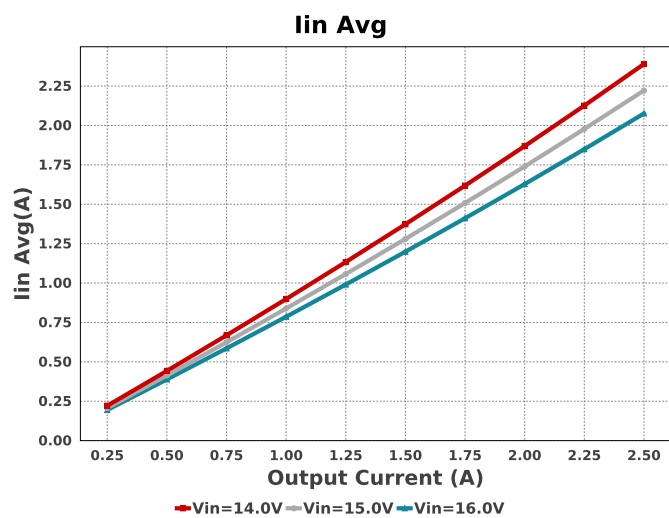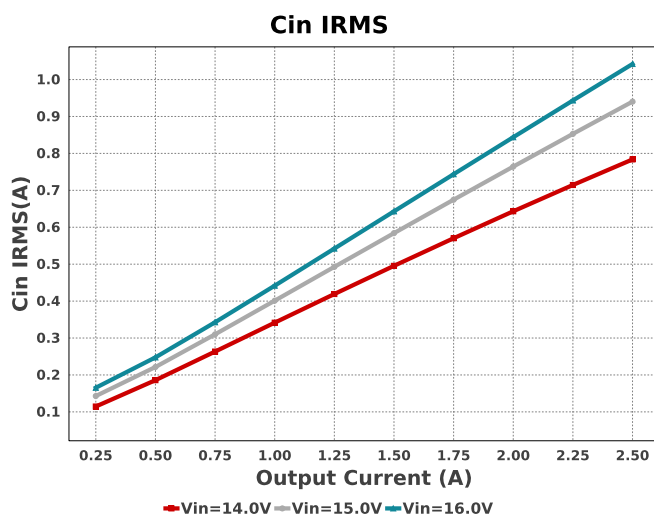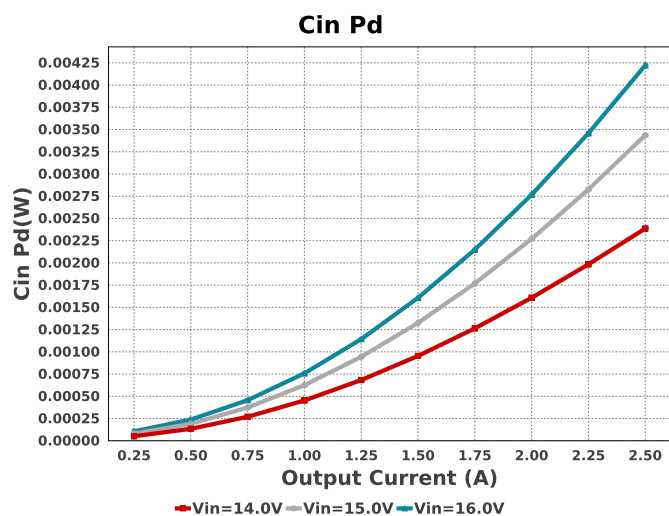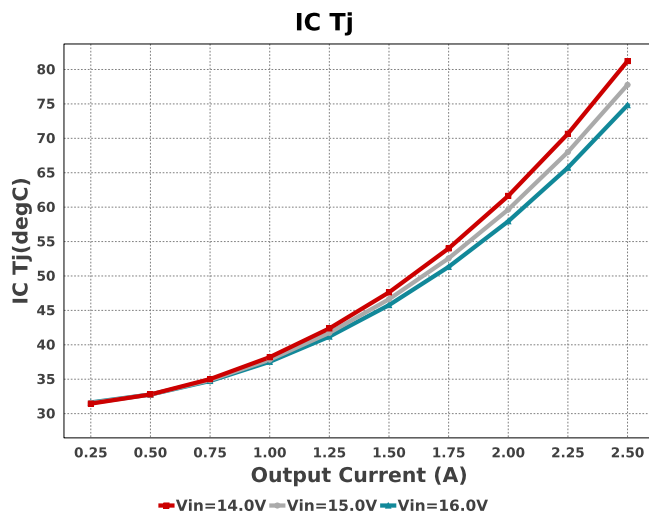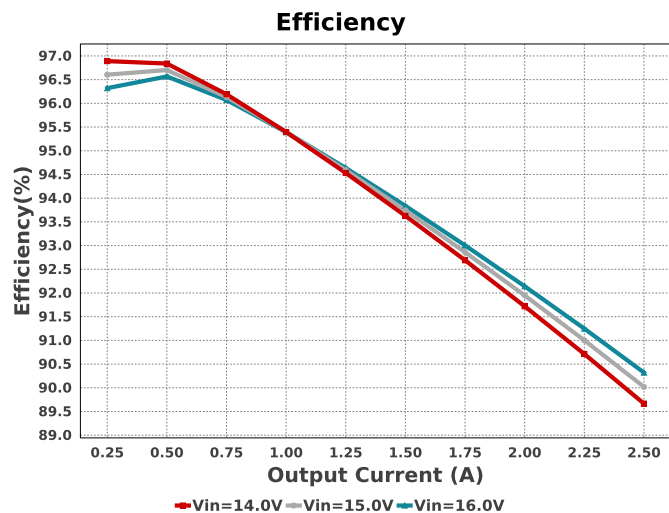

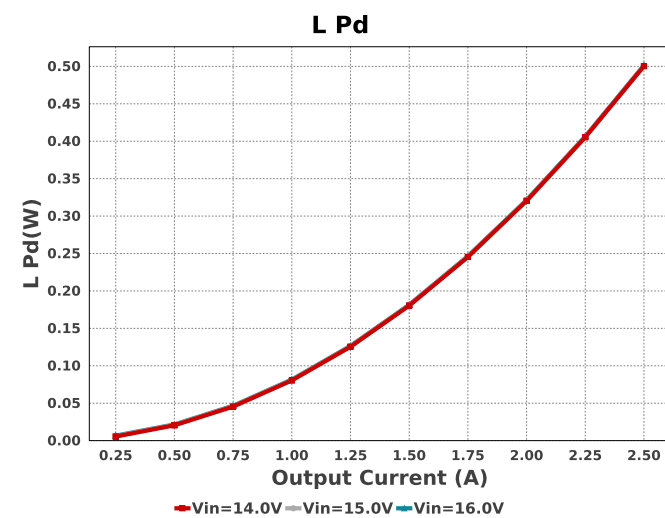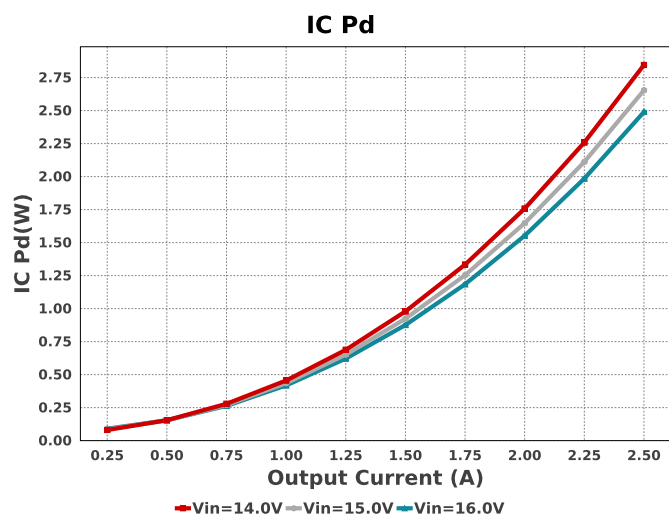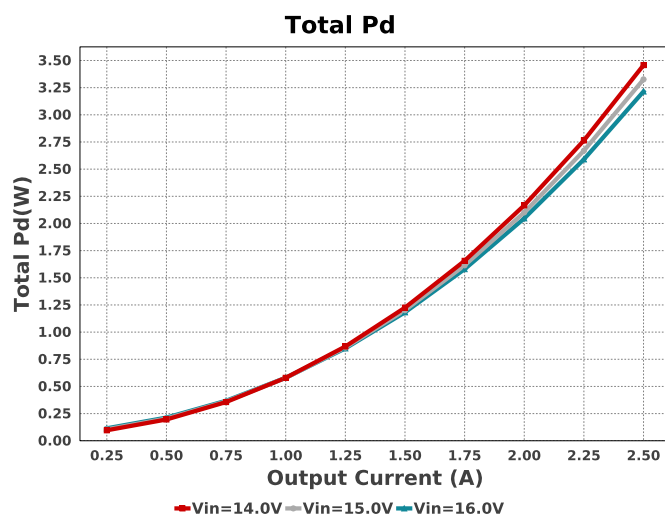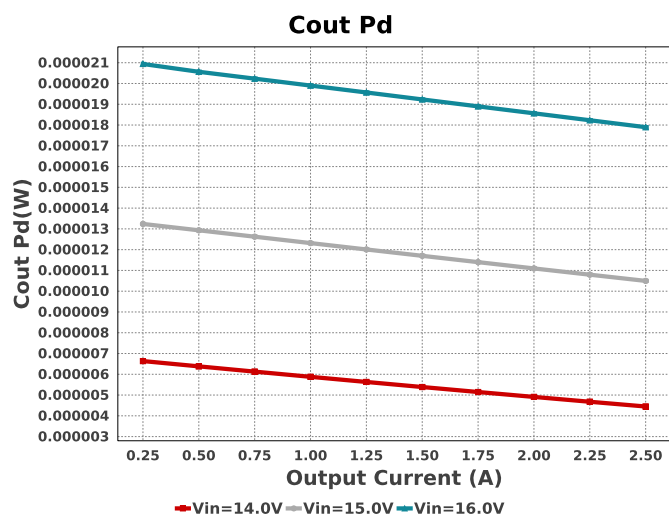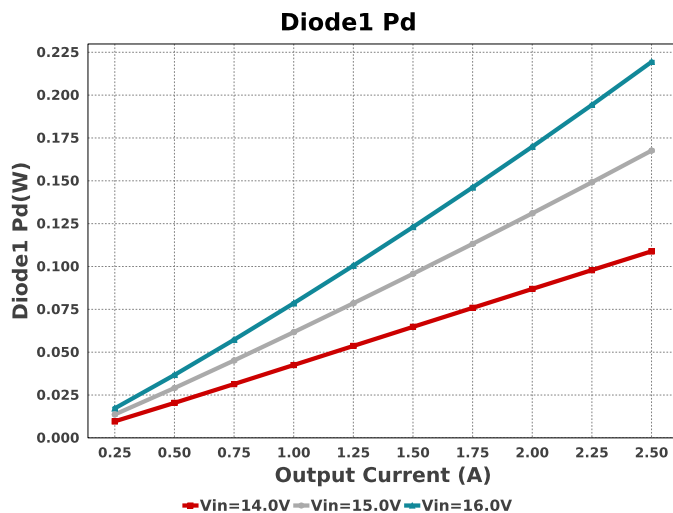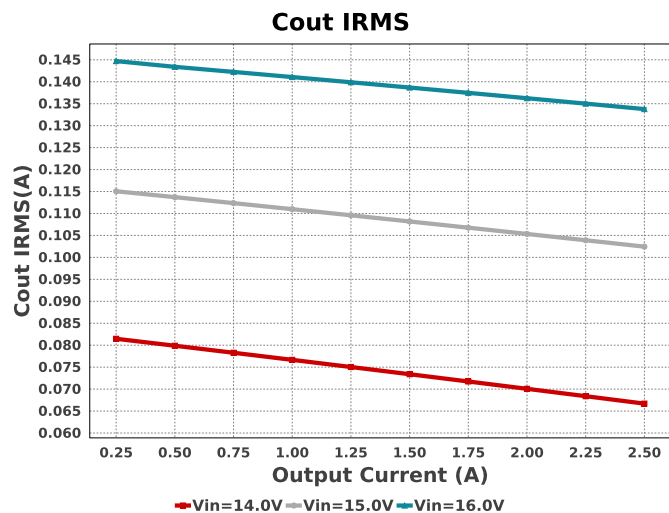

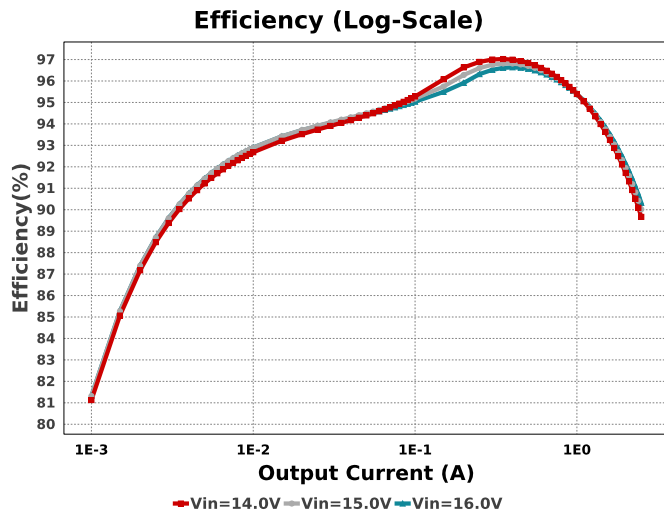

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.042 A	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	4.221 mW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	133.777 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	17.896 $\mu$ W	Capacitor	Output capacitor power dissipation
5.	Diode1 Pd	219.36 mW	Diode	Diode1 power dissipation
6.	IC Pd	2.49 W	IC	IC power dissipation
7.	IC Tj	74.814 degC	IC	IC junction temperature
8.	IC Tolerance	19.0 mV	IC	IC Feedback Tolerance
9.	ICThetaJA	18.0 degC/W	IC	IC junction-to-ambient thermal resistance
10.	Iin Avg	2.076 A	IC	Average input current
11.	Ipp percentage	18.537 %	Inductor	Inductor ripple current percentage (with respect to average inductor current)
12.	L Ipp	463.416 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	501.43 mW	Inductor	Inductor power dissipation
14.	Cin Pd	4.221 mW	Power	Input capacitor power dissipation
15.	Cout Pd	17.896 $\mu$ W	Power	Output capacitor power dissipation
16.	Diode1 Pd	219.36 mW	Power	Diode1 power dissipation
17.	IC Pd	2.49 W	Power	IC power dissipation
18.	L Pd	501.43 mW	Power	Inductor power dissipation
19.	Total Pd	3.215 W	Power	Total Power Dissipation
20.	BOM Count	14	System	Total Design BOM count
21.	Duty Cycle	78.011 %	System	Duty cycle
22.	Efficiency	90.321 %	System	Steady state efficiency
23.	FootPrint	376.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
24.	Frequency	271.739 kHz	System	Switching frequency
25.	Iout	2.5 A	System	Iout operating point
26.	Mode	CCM	System	Conduction Mode
27.	Pout	30.0 W	System	Total output power
28.	Total BOM	\$2.59	System	Total BOM Cost
29.	Vin	16.0 V	System	Vin operating point
30.	Vout	12.0 V	System	Operational Output Voltage
31.	Vout Actual	12.094 V	System	Vout Actual calculated based on selected voltage divider resistors
32.	Vout Tolerance	3.432 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
33.	Vout p-p	10.451 mV	System	Peak-to-peak output ripple voltage

## Design Inputs

Name	Value	Description
Iout	2.5	Maximum Output Current
VinMax	16.0	Maximum input voltage
VinMin	14.0	Minimum input voltage
Vout	12.0	Output Voltage
base_pn	LM5012	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

## WEBENCH® Assembly

### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of  $C_{in}$  and  $C_{out}$ , and the inductance and DC resistance of  $L1$  before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

### Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 14.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to  $V_{in}$  and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from  $V_{out}$  and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between  $V_{in}$  and GND, a load is connected between  $V_{out}$  and GND and a current meter is connected in series between  $V_{out}$  and the load. The load must be able to handle at least rated output power + 50% ( 7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



### Design Assistance

1. Master key : B6A26D6A3E7E6C6A58AACF63601B9E73[v1]
2. **LM5012** Product Folder : <http://www.ti.com/product/LM5012> : contains the data sheet and other resources.

**Important Notice and Disclaimer**

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.